 


# 이산수학

## Discrete Mathematics




### Chapter 11:

### 부울대수와 논리 게이트

Soongsil University : Kim Chang Wook




Lecture Note : *Digital Design*, with RTL Design, VHDL, and Verilog, 2nd Edition, by Frank Vahid,  
**Discrete Mathematics and Its Applications**, 7E By Kenneth H. Rosen

# Boolean Algebra (부울 대수)

 

- Founder: Digital computer and digital circuit design theory
- 1938, 22 year old at MIT, wrote master's thesis describing how Boolean algebra could be applied to switch-based circuit.

   - 1854년 영국의 수학자 George Boole이 “The Laws of Thought” 에서 수학적 논리 규칙으로 처음 소개
- 1938년 Shannon이 부울 대수의 기본 개념을 이용하여 회로를 설계하는데 사용할 수 있음을 증명
- 0과 1의 조합으로 연산되는 것을 **부울 대수**라고 함
- 컴퓨터나 디지털 전자 장치는 0, 1 두 가지 상태를 갖는 기본 장치로 구성
- 스위치나 회로는 ON과 OFF의 두 상태 중 하나인 1(T) or 0(F) 으로 표현
- 논리회로에서 Positive Logic에서는 “0”은 낮은 전압대를, “1”은 높은 전압대를 표현.




**부울 변수는 단지 두 개의 서로 다른 값을 갖는다.**

# Boolean Algebra : Basic Operations



## 부울대수의 기본 연산: AND, OR, NOT( Complementation )
 
### ◆ NOT 연산( Boolean Complementation : 부울 보수 )

- 표기 :  $A'$  또는  $\bar{A}$
- 2진 변수값을 반전시키는 단항 연산자.  
 $0' = \bar{0} = 1$        $1' = \bar{1} = 0$
- NOT 연산을 하면 부울변수  $x$ 의 값이 0인 경우 1, 1의 경우 0이 된다.
- 논리 게이트 : Inverter or NOT Gate
- 낮은 입력 전압은 높은 출력 전압으로 나타난다.



x	F
0	1
1	0

  

# Boolean Algebra : Basic Operations

## ◆ AND 연산 (Boolean Multiplication: 부울곱)

- 표기 :  $A \cdot B$  또는  $AB$

일반적으로,  $A \cdot B$  대신  $AB$  로 표기한다.


- 2진 변수의 값을 곱하는 이항 연산자

$$: 0 \cdot 0 = 0 \quad 0 \cdot 1 = 0 \quad 1 \cdot 0 = 0 \quad 1 \cdot 1 = 1$$




- AND 연산은 부울 변수  $x$ 와  $y$ 가 1일 때만 1이다.

- 논리 게이트 : AND Gate

 - $x$ 와  $y$ 가 1일 때  $F$ 가 1 이 되며, 출력은 높은 전압,  
 $x$  와  $y$  중에서 하나라도 0이면  $F$ 가 0이 되며,  
출력은 낮은 전압으로  
나타난다.




x	y	F
0	0	0
0	1	0
1	0	0
1	1	1

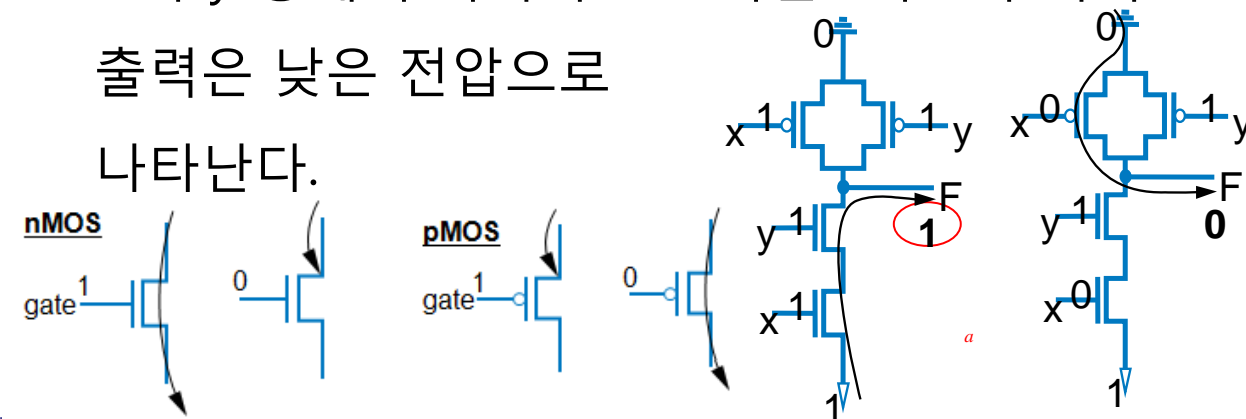  



# Boolean Algebra : Basic Operations
 
## ◆ OR 연산(Boolean Addition : 부울합)


- 표기 :  $A + B$
- 논리 게이트 : OR Gate
- x 또는 y가 1일 때  $F=1$ 이 되며,  
x와 y가 0일 때  $F$ 가 0이 되며,  
출력은 낮은 전압으로 나타난다.




x	y	F
0	0	0
0	1	1
1	0	1
1	1	1

  


# More Gates

 


x	y	F
0	0	1
0	1	1
1	0	1
1	1	0

 

x	y	F
0	0	1
0	1	0
1	0	0
1	1	0

 

x	y	F
0	0	0
0	1	1
1	0	1
1	1	0

 

x	y	F
0	0	1
0	1	0
1	0	0
1	1	1

- NAND : Opposite of AND (“NOT AND”),  $F=(ab)'$
- NOR : Opposite of OR (“NOT OR”),  $F=(a+b)'$
- XOR : “exclusive OR”, Exactly 1 input is 1,  
For 2-input XOR. variables  $a$  and  $b$  :  $F= a'b+ab'= a \oplus b$   
For more inputs -- odd number of 1s three variables :  $F= a \oplus b \oplus c$
- XNOR: “exclusive nor”, Opposite of XOR (“NOT XOR”) :  $F= a'b'+ab= a \odot b$   
 $= (a \oplus b)'$

# Boolean Algebra Terminology

❖ Example equation :  $F(a,b,c) = a'bc + abc' + ab + c$

## ❖ *Variable* (변수)

- Represents a value (0 or 1)
- Above equation has three variables: a, b, and c

## ❖ *Literal* (문자)

- Appearance of a variable, in true or complemented form
- Nine literals:  $a'$ ,  $b$ ,  $c$ ,  $a$ ,  $b$ ,  $c'$ ,  $a$ ,  $b$ , and  $c$   
Ex)  $ab'c + a'b + a'bc' + b'c'$  : 모두 10개의 문자로 구성

## ❖ *Product term*

- Product of literals
- Four product terms:  $a'bc$ ,  $abc'$ ,  $ab$ ,  $c$

## ❖ *Sum-of-products*

- Equation written as OR of product terms only
- sum-of-products form :  $F = a + b' + ac$        $F = a'bc + abc' + ab + c$
- Following equations are not in sum-of-products form.

$$F = (a+b)c \quad F = (a')' + b \quad "F = (a+b)c + d"$$

# Logic Gates

## ❖ LOGIC GATES

1. Boolean Algebra is used to **model circuitry of electronic devices**.
2. Each circuit is designed **using the rules of Boolean Algebra**.
3. The **basic elements of circuits** are called ***gates*** (게이트).
4. Each type of gate implements a Boolean operation.
5. The circuits give **output that depends only on the input**.
6. Circuits **have no memory** capabilities.

❖ These circuits are called ***combinational circuits***(조합회로)  
***Combinational circuit*** : Output depend solely on the present combination of the circuit inputs' values.

***Sequential circuit*** : Output depend on the present and past input values.

❖ We will construct combinational circuits using three types of elements. .Inverter, OR gate, AND gate





# Boolean Expressions and Truth

- 부울식은 하나 또는 둘 이상의 부울 변수(A, B, X, Y 등)와 상수( 0또는 1) 그리고 기본 연산(AND, OR, NOT)으로 구성된 식이다.

(예 1) 가장 간단한 부울식은 단 하나의 부울 변수나 상수로만 구성된 식:  $B'$

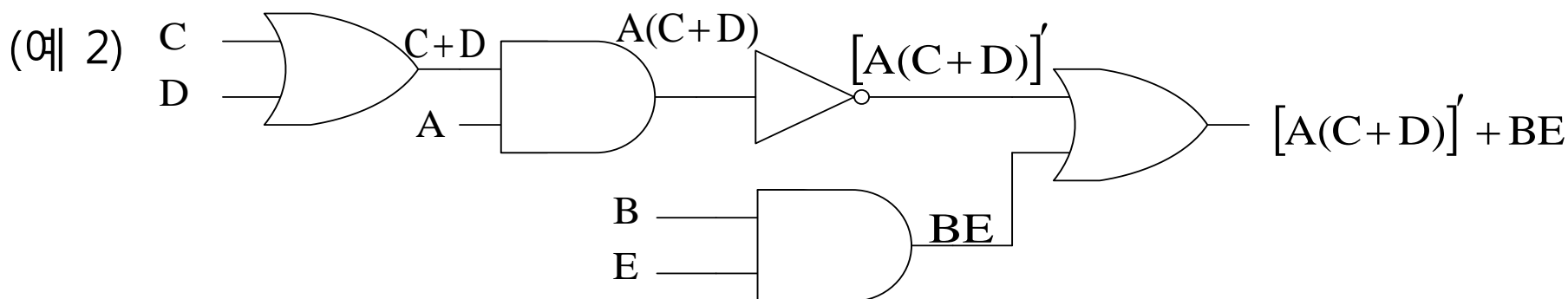 $AB' + C$ 식에서 ①부울 변수 B의 보수화가 먼저 실행되고, ②부울변수 A와 AND 연산을 한다. 그리고 마지막으로 ③부울변수 C와 OR연산의 순서로 진행된다.



$$A=B=C=1 \text{ 이고, } D=E=0 \text{ 이면 부울식의 최종값은 } [A(C+D)]' + BE = [1(1+0)]' + 1 \cdot 0 = [1 \cdot 1]' + 0 = 0 + 0 = 0$$

# Basic Theorems Tables

**TABLE 5** Boolean Identities.

<i>Identity</i>	<i>Name</i>
$\overline{\overline{x}} = x$	Law of the double complement
$x + x = x$ $x \cdot x = x$	Idempotent laws 멍등법칙
$x + 0 = x$ $x \cdot 1 = x$	Identity laws 항등법칙
$x + 1 = 1$ $x \cdot 0 = 0$	Domination laws 지배법칙
$x + y = y + x$ $xy = yx$	Commutative laws 교환법칙

<i>Identity</i>	<i>Name</i>
$x + (y + z) = (x + y) + z$ $x(yz) = (xy)z$	Associative laws 결합법칙
$x + yz = (x + y)(x + z)$ $x(y + z) = xy + xz$	Distributive laws 분배법칙
$\overline{(xy)} = \bar{x} + \bar{y}$ $\overline{(x + y)} = \bar{x} \bar{y}$	De Morgan's laws 드모르간의 법칙
$x + xy = x$ $x(x + y) = x$	Absorption laws 흡수법칙
$x + \bar{x} = 1$	Unit property 단위 성질
$x\bar{x} = 0$	Zero property 제로 성질

# Commutative, Associative, and Distributive Laws

- 둘 또는 그 이상의 부울변수들이 모두 OR 연산인 경우

변수들 중에서 어느 한 변수가 1이면 결과 값은 1.

모든 변수들이 0이면 OR 연산의 결과는 0이다.

$$X + XY + XZ = X(1 + Y + Z) = X, \quad X = Y = Z = 0 \text{ 일때 } X + Y + Z = 0$$

- 부울대수에서의 분배법칙(제1법칙)

$$X(Y + Z) = XY + XZ$$

- 부울대수에서의 분배법칙(제2법칙)

$$X + (YZ) = (X + Y)(X + Z)$$

증명)  $(X + Y)(X + Z) = (X + Y)X + (X + Y)Z$

$$= XX + XY + XZ + YZ$$

$$= X + XZ + XY + YZ$$

$$= X \cdot 1 + XZ + XY + YZ$$

$$= X(1 + Z + Y) + YZ$$

$$= X + YZ$$

# Simplification Theorems

## ◆ 부울대수에서의 간략화 법칙

$$XY + XY' = X \quad (\text{증명}) \quad XY + XY' = X(Y + Y') = X$$

$$(X + Y)(X + Y') = X \quad (\text{증명}) \quad (X + Y)(X + Y') = X + X(Y + Y') + (YY') \\ = X + 0 = X$$

$$X + XY = X \quad (\text{증명}) \quad X + XY = X \cdot 1 + XY = X(1 + Y) = X$$

$$X(X + Y) = X \quad (\text{증명}) \quad X(X + Y) = XX + XY = X + XY = X$$

$$(X + Y')Y = XY \quad (\text{증명}) \quad (X + Y')Y = XY + Y'Y = XY + 0 = XY$$


$$XY' + Y = X + Y \quad (\text{증명}) \quad XY' + Y = (X + Y)(Y' + Y) = X + Y$$

# Simplification Theorems


- 간략화 정리는 어떤 부울식을 더 간단한 부울식으로 대체될 수 있다는 것을 의미한다. 디지털 시스템에서 시스템을 나타내는 부울식은 논리 게이트로 구현되기 때문에 부울식을 간략화 한다는 것은 **부울식을 나타내는 논리 게이트 수를 감소시켜 비용적인 이득**을 볼 수 있다는 장점이 있다.

✓ 예1)

$$F = A(A' + B)$$

 

$$F = A(A' + B) = AA' + AB = AB$$

 

✓ 예2-4) 간략화

$$(1) Z = A'BC + A' = A'BC + A' \cdot 1 = A'(BC + 1) = A'$$

$$(2) Z = [A + B'C + D + EF][A + B'C + (D + EF)']$$

$$Z = [X + Y][X + Y'] = XX + X(Y + Y') + YY' = X = A + B'C$$

$$(3) Z = (AB + C)(B'D + C'E') + (AB + C)'$$

$$Z = Y'X + Y = (X + Y)(Y' + Y) = X + Y = (B'D + C'E') + (AB + C)'$$

# Representations of Boolean Functions

Boolean function : mapping of each possible combination of values for the function's variables(input) to either 0 or 1(output)


(b)

Equation 1:  $F(a,b) = a'b' + a'b$


Equation 2:  $F(a,b) = a'$

English 1: F outputs 1 when a is 0 and b is 0, or when a is 0 and b is 1.

English 2: F outputs 1 when a is 0, regardless of b's value

 

Circuit 1

 

Circuit 2

a	b	F
0	0	1
0	1	1
1	0	0
1	1	0

Truth table

(d)

The function F

- Circuit may represent an actual physical implementation of a Boolean function.
- Different circuit can represent same function.
- Advantage :circuit can enable quick and easy comprehension of a function by humans

## ❖ A function can be represented in different ways

- Each representation has its own advantages and disadvantages,
- each is useful at different times during design
- Above shows seven representations of the same functions  $F(a,b)$ ,
- using four different methods: English, Equation, Circuit, and Truth Table

# Truth Table Representation of Boolean Functions

❖ Input variables shows all possible value combinations of those inputs.

진리표는 부울식에 있는 부울 변수들 값의 가능한 모든 조합에 대한 부울식의 값을 나타낸다.


❖ Define value of F for each possible combination of input values

n-변수 식의 진리표는  $2^n$  개의 행으로 나타난다.

- 2-input function: 4 rows (a)
- 3-input function: 8 rows (b)
- 4-input function: 16 rows (c)
- $2^n$

❖ Unlike equations and circuits, a Boolean function has **only one truth table representation**.

 ❖ Ex) 디지털회로에서 진리표 작성  
두변수 : AB  $\rightarrow 2^2=4$  rows



a	b	F
0	0	
0	1	
1	0	
1	1	

(a)

a	b	c	F
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

(b)

a	b	c	d	F
0	0	0	0	
0	0	0	1	
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	
0	1	1	0	
0	1	1	1	
1	0	0	0	
1	0	0	1	
1	0	1	0	
1	0	1	1	
1	1	0	0	
1	1	0	1	
1	1	1	0	
1	1	1	1	

(c)

A	B	A'	F = A' + B
0	0	1	1
0	1	1	1
1	0	0	0
1	1	0	1



# Converting among Boolean Function Representations

- Can convert from any representation to another


## ❖ Common conversions

### 1. Equation to circuit



- AND, OR, NOT  $\rightarrow$  AND gate, OR gate, NOT gate
 
### 2. Circuit to equation

- Start at inputs, write expression of each gate output
- $F(c,h,p)=c'(h+p)$



  Ex) 1.  $f(x,y)=(x+y')(x'+y) \rightarrow$  논리 회로 구성.    2. 논리회로  $\rightarrow$  부울 식



# Converting among Representations

## ❖ More common conversions

4. Truth table to equation (which we can then convert to circuit)


- Creating a product term for each 1 in the output, then ORing all the product.

3. Equation to truth table

- First creating a truth table structure appropriate for the number of input variables, then evaluating the right-hand side of the eq. for each input values.
- Creating intermediate columns helps

(3) Convert to truth table:  $F = a'b' + a'b$

Inputs				Output
a	b	$a'b'$	$a'b$	F
0	0	1	0	1
0	1	0	1	1
1	0	0	0	0
1	1	0	0	0

 

Inputs		Outputs	Term
a	b	F	F = sum of
0	0	1	$a'b'$
0	1	1	$a'b$
1	0	0	
1	1	0	

(4)  $F = a'b' + a'b$



a	b	c	F	
0	0	0	0	
0	0	1	0	
0	1	0	0	
0	1	1	0	
1	0	0	0	
1	0	1	1	$ab'c$
1	1	0	1	$abc'$
1	1	1	1	$abc$

(4)  $F = ab'c + abc' + abc$

# Converting among Representations
  
## 5. Converting from Circuit to Truth Table

- First convert to circuit to equation, then equation to table
  - Starting from the gates closest to inputs, label each gate's output as an expression of the gate's inputs.
  - Finally, label the rightmost AND gate's output  $F$



Inputs						Outputs
a	b	c	ab	(ab)'	c'	$F=(ab)'c'$
0	0	0	0	1	1	1
0	0	1	0	1	0	0
0	1	0	0	1	1	1
0	1	1	0	1	0	0
1	0	0	0	1	1	1
1	0	1	0	1	0	0
1	1	0	1	0	1	0
1	1	1	1	0	0	0

### Truth Table

→ equation

$$\begin{aligned}
 F &= a'b'c' + a'bc' + ab'c' \\
 &= c'(a'b' + a'b + ab') \\
 &= c'(a'(b' + b) + ab') \\
 &= c'(a' + ab') \\
 &= c'(a' + a)(a' + b') \\
 &= c'(a' + b') \\
 &= c'(ab)' \\
 &= (ab)'c'
 \end{aligned}$$

- Distributive

$$a * (b + c) = ab + ac$$

$$a + (bc) = (a+b)(a+c)$$

- Identity

$$0 + a = a + 0 = a$$

$$1 * a = a * 1 = a$$

- Complement

$$a + a' = 1$$

$$a * a' = 0$$

- DeMorgan's Law

$$(a+b)' = a'b'$$

$$(ab)' = a' + b'$$

# Standard Representation: Truth Tables

❖ For any Boolean function

: many possible equations and circuits, but only one truth table

→ Truth tables represent a standard representation of a function, unique

❖ How can we determine if two functions are the same?

- Solution: Convert to truth tables

- : Only ONE truth table representation of a given function - **Standard** representation

- Comparing truth tables works fine when a function has only 2 inputs

- If a function has many inputs  $n \rightarrow$  truth table's number of rows  $2^n$  grows very quickly. We can't realistically expect to compare 2 tables

- The number of output 1s in a truth table may be very small compared to the number of output 0s → Is there a more compact but still standard representation of a Boolean function ?

# Canonical Form – Sum of Minterms Equations

- ❖ Truth tables too big for numerous inputs
- ❖ Use standard form of a Boolean equation that function outputs 1
  - Known as **canonical form**
  - One canonical form for Boolean function : sum of minterms
  - Minterm** : product term whose literals include every variable of the function exactly once, in true or complemented form
  - Converting step : any equation to sum-of-minterms canonical form
    - Manipulate the equation until it is in sum-of-products form
    - Then expand each term until all terms are minterms
    - Arrange the literals (alphabetical) and the terms in the order (truth table)

Ex: Determine if  $F1 = (a+b)(a'+ac)b$  is equivalent to  $F2 = a'bc' + a'bc + abc$ ,  
by converting first equation to canonical form (second already is)

$$\begin{aligned} F1 &= (a+b)(a'+ac)b = aa'b + aacb + ba'b + bacb = acb + a'b && \text{(sum of products)} \\ &= abc + a'b(c+c') = abc + a'bc + a'bc' && (a+a'=1 \quad aa'=0 \quad \text{적용}) \\ &= a'bc' + a'bc + abc \quad \text{(arrange: truth table)} \Rightarrow \text{Equivalent } F1=F2 \end{aligned}$$

# Canonical Form – Sum of Minterms

Ex: Determine whether the functions  $G$  and  $H$  are equivalent.

$$G(a,b,c,d,e) = abcd + a'bcde \quad \text{and}$$

$$H(a,b,c,d,e) = abcde + abcde' + a'bcde + a'bcde(a' + c)$$

$$G = abcd + a'bcde$$

$$G = abcd(e+e') + a'bcde$$

$$G = abcde + abcde' + a'bcde$$

$$G = a'bcde + abcde' + abcde \quad (\text{sum of minterms form})$$

expand each term until all terms are minterms  
: complement property  $a+a'=1$

Equivalent

$$H = abcde + abcde' + a'bcde + a'bcde(a' + c)$$

$$H = abcde + abcde' + a'bcde + a'bcdea' + a'bcdec$$

$$H = abcde + abcde' + a'bcde + a'bcde + a'bcde$$

$$H = abcde + abcde' + a'bcde$$

$$H = a'bcde + abcde' + abcde$$

Checking the equivalence using truth tables :  $32(2^5)$  rows each  
Using sum of minterms was more appropriate.

# Canonical Form – Sum of Minterms Equations

❖ Ex: Find the sum-of-products expansion for the function

$$F(x, y, z) = (x + y)z' = xz' + yz' \quad : \text{Distributive law}$$

$$= x1z' + 1yz' \quad : \text{Identity law}$$

$$= x(y + y')z' + (x + x')yz' \quad : \text{Unit property}$$

$$= xyz' + xy'z' + xyz' + x'yz' \quad : \text{Distributive law}$$

$$= x'yz' + xy'z' + xyz' \quad : \text{Idempotent law}$$

$x$	$y$	$z$	$x + y$	$\bar{z}$	$(x + y)\bar{z}$
1	1	1	1	0	0
1	1	0	1	1	1
1	0	1	1	0	0
1	0	0	1	1	1
0	1	1	1	0	0
0	1	0	1	1	1
0	0	1	0	0	0
0	0	0	0	1	0

## Maxterms

- Boolean product of Boolean sums (**maxterms**) : correspond to those combinations of values for which the function has the value 0.
- The resulting expansion is called the product-of-sums expansion.
- A maxterm is the standard sum.  
A maxterm has the value 0 for one and only combination of values of its variables.
- A minterm is the complement of a maxterm.
- To get the **maxterms**
  - Take the complement.
  - Obtain the **sum of minterms**.
  - Complement both sides of the **sum of minterms** obtained in (2)
- Boolean functions expressed as a **sum of minterms** or **product of maxterms**, are said to be in **canonical form**.

	Minterms	Maxterms
$x y z$	Term	Term
0 0 0	$x'y'z'$	$x+y+z$
0 0 1	$x'y'z$	$x+y+z'$
0 1 0	$x'yz'$	$x+y'+z$
0 1 1	$x'yz$	$x+y'+z'$
1 0 0	$xy'z'$	$x'+y+z$
1 0 1	$xy'z$	$x'+y+z'$
1 1 0	$xyz'$	$x'+y'+z$
1 1 1	$xyz$	$x'+y'+z'$



# Minterm and Maxterm Expansions

## ❖ 최소항(minterm)

- 일반적으로  $n$  변수의 최소항은 각 변수가 그대로 혹은 보수 형태로 한번씩만 나타나는  $n$  개의문자의 곱.  $F=A'BC+AB'C'+AB'C+ABC'$

## ❖ 최대항(maxterm)

- 일반적으로  $n$  변수의 최대항은 각 변수가 그대로 혹은 보수 형태로 한번씩만 나타나는  $n$  개의문자의 합.  $F=(A+B+C)(A+B+C')(A+B'+C)$

❖최소항(최대항)은 다음과 같은 간단한 형태로 표현 가능하다.

행번호	A	B	C	최소항	최대항
0	0	0	0	$A'B'C' = m_0$	$A + B + C = M_0$
1	0	0	1	$A'B'C = m_1$	$A + B + C' = M_1$
2	0	1	0	$A'BC' = m_2$	$A + B' + C = M_2$
3	0	1	1	$A'BC = m_3$	$A + B' + C' = M_3$
4	1	0	0	$AB'C' = m_4$	$A' + B + C = M_4$
5	1	0	1	$AB'C = m_5$	$A' + B + C' = M_5$
6	1	1	0	$ABC' = m_6$	$A' + B' + C = M_6$
7	1	1	1	$ABC = m_7$	$A' + B' + C' = M_7$



# Minterm and Maxterm Expansions

- $f$ 의 최소항 혹은 최대항 전개가 주어지면  $f'$ 에 대한 최소항 혹은 최대항 전개는 쉽게 구해질 수 있다.
- $f$ 가 0일 때  $f'$ 은 1이 되며,  $f'$ 에 대한 최소항 전개는  $f$ 의 최소항 전개에서 제외된 최소항을 열거하면 쉽게 얻을 수 있다.

$$f = A'BC + AB'C' + AB'C + ABC' + ABC$$

$$f(A, B, C) = m_3 + m_4 + m_5 + m_6 + m_7$$

$$f(A, B, C) = \sum m(3, 4, 5, 6, 7)$$

$$f'(A, B, C) = \sum m(0, 1, 2)$$

- 마찬가지로  $f'$ 의 최대항 전개는  $f$ 에 없는 최대항을 포함하여 구할 수 있다.

$$f(A, B, C) = \prod M(0, 1, 2)$$

$$f'(A, B, C) = \prod M(3, 4, 5, 6, 7)$$

# Multiplying Out and Factoring

## ◆ 논리합의 곱(Product of Sum) 형식

$$X + YZ = (X + Y)(X + Z)$$


논리곱의 합 부울 함수를 논리합의 곱형태로 인수화. 분배제2법칙

$$(1) A + B'CD = (A + B')(A + CD) = (A + B')(A + C)(A + D)$$


$$(2) AB' + C'D = (AB' + C')(AB' + D) = (A + C')(B' + C')(A + D)(B' + D)$$

$$(3) C'D + C'E' + G'H = C'(D + E') + G'H = (C' + G'H)(D + E' + G'H) \\ = (C' + G')(C' + H)(D + E' + G')(D + E' + H)$$

 - 논리곱의 합식을 논리 게이트로 표시할 때 하나 이상의 AND 게이트가 입력단이 되고, 이 AND 게이트의 출력들이 OR 게이트의 입력이 되는 형태를 구성한다.
- 논리합의 곱식을 논리 게이트로 표시할 때 하나 이상의 OR 게이트가 입력단이 되고, 이 OR 게이트의 출력들이 AND 게이트의 입력이 되는 형태를 구성한다.



논리곱의 합식의 논리 게이트 표현

 

논리합의 곱식의 논리 게이트 표현

# DeMorgan's Laws

❖ DeMorgan의 정리 :  $(X+Y)'=X'Y'$   $(XY)'=X'+Y'$

진리표에 의한 DeMorgan의 증명

$X$	$Y$	$X'$	$Y'$	$X+Y$	$(X+Y)'$	$X'Y'$	$XY$	$(XY)'$	$X'+Y'$
0	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	0	0	1	1
1	0	0	1	1	0	0	0	1	1
1	1	0	0	1	0	0	1	0	0

◆  $n$  변수에 대한 DeMorgan의 정리

$$(X_1 + X_2 + X_3 + \cdots + X_n)' = X_1' X_2' X_3' \cdots X_n' \quad (2-23)$$

$$(X_1 X_2 X_3 \cdots X_n)' = X_1' + X_2' + X_3' + \cdots + X_n' \quad (2-24)$$

예)

$$(1) [(A' + B)C']' = (A' + B)' + C = AB' + C$$

$$\begin{aligned}
 (2) [(AB' + C)D' + E']' &= [(AB' + C)D']' E \\
 &= [(AB' + C)' + D]E = [(AB')' C' + D]E = [(A' + B)C' + D]E
 \end{aligned}$$

# DeMorgan's Laws

❖  $(a+b)' = a'b'$

- Proof 1

$$(a+b) + (a+b)' = 1 \quad \text{if } (a+b) + a'b' = 1 \text{ then } (a+b)' = a'b'$$
$$(a+b) + a'b' = (a+b+a')(a+b+b') = (1+b)(a+1) = 1 \rightarrow (a+b)' = a'b'$$

- Proof 2

$$(a+b)(a+b)' = 0 \quad \text{if } (a+b)(a'b') = 0 \text{ then } (a+b)' = a'b'$$
$$(a+b)(a'b') = aa'b + ba'b' = 0b + 0a' = 0 \rightarrow (a+b)' = a'b'$$

❖  $(ab)' = a' + b'$

- Proof 1

$$(ab) + (ab)' = 1 \quad \text{if } (a' + b') + (ab) = 1 \text{ then } (ab)' = a' + b'$$
$$(a' + b') + (ab) = (a' + b' + a)(a' + b' + b) = (1 + b')(a' + 1) = 1 \rightarrow (ab)' = a' + b'$$

- Proof 2

$$(ab)(ab)' = 0 \quad \text{if } (ab)(a' + b') = 0 \text{ then } (ab)' = a' + b'$$
$$(ab)(a' + b') = aba' + abb' = 0b + 0a' = 0 \rightarrow (ab)' = a' + b'$$


Complement Property :  $a + a' = 1$        $aa' = 0$

# Exclusive-OR and Equivalence Operations

## ❖ Exclusive-OR의 진리표

$X$	$Y$	$X \oplus Y$
0	0	0
0	1	1
1	0	1
1	1	0


$$X \oplus Y = X'Y + XY'$$

 

## Exclusive-NOR(XNOR) 진리표

$X$	$Y$	$F$
0	0	1
0	1	0
1	0	0
1	1	1

$$(X \odot Y) = XY + X'Y'$$

 

## ❖ Exclusive-OR에 대한 정리

$$X \oplus 0 = X \quad X \oplus 1 = X' \quad X \oplus X = 0 \quad X \oplus X' = 1 \quad X \oplus Y = Y \oplus X$$

$$(X \oplus Y) \oplus Z = X \oplus (Y \oplus Z) = X \oplus Y \oplus Z$$

$$\begin{aligned} (X \oplus Y) \oplus Z &= (XY' + X'Y)Z' + (XY' + X'Y)'Z = XY'Z' + X'YZ' + (XY')'(X'Y)'Z = // + (X' + Y)(X + Y')Z \\ &= (XY' + X'Y)Z' + (X'Y' + XY)Z = X'(YZ' + Y'Z) + X(Y'Z' + YZ) = X \oplus (Y \oplus Z) \end{aligned}$$

$$XY \oplus XZ = XY(XZ)' + (XY)'XZ = XY(X' + Z') + (X' + Y')XZ$$

$$= XYX' + XYZ' + X'XZ + Y'XZ = XYZ' + Y'XZ = X(YZ' + Y'Z) = X(Y \oplus Z)$$

$$(X \oplus Y)' = (XY' + X'Y)' = ((XY')'(X'Y)') = (X' + Y)(X + Y') = XY + X'Y' = X \oplus Y' = X' \oplus Y$$

Exclusive - NOR는 Exclusive - OR의 보수이다.

$$(X \odot Y) = (X \oplus Y)' = (X'Y + XY')' = (X + Y')(X' + Y) = XX' + XY + X'Y' + Y'Y = XY + X'Y'$$

등가 및 Exclusive - OR에 대한 유용한 식 :  $(XY' + X'Y)' = XY + X'Y'$

# The Consensus Theorem

## ◆ 합의 정리

- 합의 정리는 부울식을 간소화하는데 매우 중요한 역할을 한다 .

$XY+X'Z+YZ$  형태로 주어지는 경우,

$YZ$ 는 중복되는 항으로 소거되어  $XY+X'Z$  로 표시할 수 있다.

소거된 항을 **합의 항**(Consensus term)이라고 한다.

두 항으로 된 식에서 한쪽 항에는 한 변수가, 다른 한쪽에는 그 변수의 보수가 있을 경우, 합의 항은 변수에 보수를 취한 쪽의 남은 변수와 보수를 취하지 않은 쪽의 남은 변수를 곱한 것이다.

$$ab + a'c \quad \rightarrow \quad bc$$

$$abd + b'de' \quad \rightarrow \quad adde' = ade'$$

$$ab'd + a'bd' \quad \rightarrow \quad 0$$

# The Consensus Theorem

◆ 합의 정리 :  $XY + X'Z + YZ = XY + X'Z$

$$\begin{aligned}\text{증명) } XY + X'Z + YZ &= XY + X'Z + (X + X')YZ = XY + XYZ + X'Z + X'YZ \\ &= XY(1 + Z) + X'Z(1 + Y) = XY + X'Z\end{aligned}$$

$$\text{예) } a'b' + ac + bc' + b'c + ab = a'b' + ac + bc'$$

$$\text{예제 } A'C'D + A'BD + BCD + ABC + ACD' = A'C'D + A'BD + ABC + ACD'$$

$$A'BD + BCD + ABC = A'BD + ABC + ABCD + A'BCD = A'BD(1 + C) + ABC(1 + D)$$

=  $A'BD + ABC$ 로 BCD항을 합의 정리에 의해서 소거한 경우이다.

그러나 경우에 따라서 이 항을 소거하지 않고, 이 항과 결합하는 합의 항을 찾으면 다음과 같다.  $A'C'D + BCD + A'BD = A'C'D + BCD$ ,  $BCD + ABC + ACD' = BCD + ACD'$

$$A'C'D + A'BD + BCD + ABC + ACD' = A'C'D + BCD + ACD'$$

# Algebraic Simplification of Switching Expressions

- 부울대수 법칙과 정리를 사용하여 수위칭 식을 간략화하기 위한 방법
- 수식을 간략화하는 것은 게이트를 사용하여 회로를 구현할 때 게이트 수가 줄어서 회로구성 비용을 줄이기 때문에 중요하다.

## 1. 항들의 조합

- 두 항을 조합하기 위한 정리  $XY + XY' = X(Y + Y') = X$  를 이용한다

$$abc'd' + abcd' = abd'(c' + c) = abd' \quad X = abd', \quad Y = c$$

이 정리를 사용하여 항을 조합할 때, 조합되는 두 항은 반드시 같은 변수를 가져야 하고, 변수들 중의 한 변수는 한 항에 보수형태로 표현되어야 하고 다른 항은 보수가 아니어야 한다.

- 또한  $X + X = X$  이기 때문에 주어진 항은 반복할 수 있고, 둘 이상의 다른 항과 조합될 수 있다.

$$\begin{aligned} ab'c + abc + a'bc &= ab'c + abc + \underline{abc} + a'bc = ac(b' + b) + bc(a + a') = ac + bc \\ (a + bc)(d + e') + a'(b' + c')(d + e') &= YX + Y'X = (Y + Y')X = d + e' \\ [X &= d + e', \quad Y = a + bc, \quad Y' = (a + bc)' = a'(bc)' = a'(b' + c')] \end{aligned}$$





# Algebraic Simplification of Switching Expressions

## 2. 항들의 소거

- 가능하다면 중복된 항을 소거하기 위하여  $X+XY=X(1+Y)=X$  를 사용하라.

그리고 나서 임의의 합의항을 소거하기 위해 합의항의 정리를 적용해 보라.

$$a'b + a'bc = a'b(1+c) = a'b \quad [X = a'b]$$

$$a'bc' + bcd + a'bd = a'bc' + bcd \quad [X = c, Y = bd, Z = a'b]$$

## 3. 문자들의 소거

- 중복된 문자를 소거하기 위하여  $X+X'Y=X+Y$  를 사용하라.

이 정리를 적용하기 전에 간단한 인수화를 먼저 하는 것이 필요하다.

$$\begin{aligned} A'B + A'B'C'D + ABCD' &= A'(B + B'C'D') + ABCD' = A'(B + C'D') + ABCD' \\ &= A'B + A'C'D' + ABCD' = B(A' + ACD') + A'C'D' \\ &= B(A' + CD') + A'C'D' = A'B + BCD' + A'C'D' \end{aligned}$$

## 4. 중복항 도입

중복항은  $XX'$  을 더하거나,  $(X+X')$  을 곱하거나,

$YZ$  를  $XY+X'Z$  에 더하거나,  $X$ 에  $XY$ 를 더하여 중복항을 도입할 수 있다.

$$\begin{aligned} WX + XY + X'Z' + WY'Z' &= WX + XY + X'Z' + WY'Z' + WZ' \\ &= WX + XY + X'Z' + WZ' = WX + XY + X'Z' \end{aligned}$$

# Combinational Logic Design Using a Truth Table

• 하나의 출력을 갖는 조합논리 스위칭회로를 설계하는 세 단계는 다음과 같다.

1. 회로에 필요한 기능을 나타내는 스위칭 함수를 구한다.
2. 함수에 대하여 간략화 된 대수식을 구한다.
3. 활용 가능한 논리소자를 사용하여 간략화 된 함수를 실현한다.


예) 3입력 / 1출력 스위칭 회로

1. 입력 A, B, C는 2진수 N의 각각 첫 번째, 두 번째, 세 번째 bit
2. 출력 f는  $N \geq 011_2$ 이면 1,  $N < 011_2$ 이면 0



$$\begin{aligned}
 f &= A'BC + AB'C' + AB'C + ABC' + ABC \\
 &= A'BC + AB'(C' + C) + AB(C' + C) \\
 &= A'BC + AB' + AB \\
 &= A'BC + A(B' + B) \\
 &= A'BC + A \\
 &= (A' + A)(BC + A) \\
 &= A + BC
 \end{aligned}$$

A	B	C	f	f'
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

 

# Examples of Truth Table Construction

예) 두개의 1비트 이진수 A와 B를 더하여 2비트 결과를 얻는 2진수 덧셈기를 설계.  
덧셈기의 두 입력은 부울변수 A와 B로, 출력 역시 2비트로 부울 변수 X와 Y로 한다.


A	B	합	
0	0	00	$(0+0=0)$
0	1	01	$(0+1=1)$
1	0	01	$(1+0=1)$
1	1	10	$(1+1=2)$



A	B	X	Y
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$X = AB$$

$$Y = A'B + AB' \\ = A \oplus B$$

 


# Introduction : Optimizations and Tradeoffs

❖ We now know how to build digital circuits


- How can we build **better** circuits?

❖ Let's consider two important design criteria

 - **Delay** – the time from inputs changing to new correct stable output
- **Size** – the number of transistors
- For quick estimation, assume
  - Every gate has delay of “1 gate-delay”
  - Every gate *input* requires 2 transistors
  - Ignore inverters



 Transforming F1 to F2 represents an **optimization**  
: Better in all criteria of interest




# Introduction : Optimizations and Tradeoffs

❖ Tradeoff : improves one criteria at the expense of another criteria

- Improves some, but worsens other, criteria of interest

 
## Optimizations

All criteria of interest  
are improved  
(or at least kept  
the same)


 
## Tradeoffs

Some criteria of interest  
are improved,  
while others are worsened



- ❖ We obviously prefer optimizations, but often must accept tradeoffs
- ❖ Some criteria commonly of interest to digital system designers include.
  - **Performance : execution time** for a computation on the system
  - **Size** : the number of transistors, or silicon area, of a digital system
  - **Power** : the energy consumed by the system per second, directly relating to both the heat generated by the system and to the battery energy consumed by computations.

# Combinational Logic Optimization and Tradeoffs

- Two-level size optimization using algebraic methods

- Goal: minimize the number of transistors of Two-level circuit (ORed AND gates)

- two-level logic size optimization
    - distinguish such optimization
      - : performance, power, other optimization
  - Though transistors getting cheaper (Moore's Law), still cost something

- Define problem algebraically

- Sum-of-products yields two levels

- $F = abc + abc'$  is sum-of-products;
    - $G = w(xy + z)$  is not.

- Transform sum-of-products equation to have *fewest literals and terms*

- Each literal and term translates to a gate input, each of which translates to about 2 transistors.
    - For simplicity, ignore inverters


## Example

$$F = xyz + xyz' + x'y'z' + x'y'z$$

$$F = xy(z + z') + x'y'(z + z')$$

$$F = xy*1 + x'y'*1$$
 
$$F = xy + x'y' \rightarrow \begin{array}{l} 4 \text{ literals} + 2 \text{ terms} \\ = 6 \text{ gate inputs} \end{array}$$



Note: Assuming 4-transistor 2-input AND/OR circuits;  
in reality, only NAND/NOR use only 4 transistors.

# Algebraic Two-Level Size Optimization

❖ Previous example showed common algebraic minimization method

- (Multiply out to sum-of-products, then...)
- Apply following as much as possible

- $a\mathbf{b} + a\mathbf{b}' = a(\mathbf{b} + \mathbf{b}') = a*1 = a$

- “*Combining terms to eliminate a variable*”

- ✓ (Formally called the “*Uniting theorem*”)

- Duplicating a term sometimes helps

- Doesn't change function

- ✓  $c + d = c + d + d = c + d + d + d + d \dots$

- Sometimes after combining terms, can combine resulting terms

❖ How did we “see” the opportunities to combine terms to eliminate a variable?

There is a **visual method to help us see opportunities to combine terms to eliminate a variable**, next section!  $\Rightarrow$  Karnaugh Maps

Ex 6.1

$$F = xy\mathbf{z} + xy\mathbf{z}' + x'y'\mathbf{z}' + x'y'\mathbf{z}$$

$$F = xy(\mathbf{z} + \mathbf{z}') + x'y'(\mathbf{z} + \mathbf{z}')$$

$$F = xy*1 + x'y'*1$$

$$F = xy + x'y'$$

Ex 6.2

$$F = x'y'z' + \mathbf{x'y'z} + x'yz$$

$$F = x'y'z' + \mathbf{x'y'z} + \mathbf{x'y'z} + x'yz$$

$$F = x'y'(z+z') + x'z(y'+y)$$

$$F = x'y' + x'z$$

Ex 6.3

$$G = xy'\mathbf{z}' + xy'\mathbf{z} + xy\mathbf{z} + xy\mathbf{z}'$$

$$G = xy'(\mathbf{z}'+\mathbf{z}) + xy(\mathbf{z}+\mathbf{z}')$$

$$G = xy' + xy \quad (\text{now do again})$$



$$G = x(\mathbf{y}'+\mathbf{y})$$

$$G = x$$

# Karnaugh Map (카르노맵) Minimum Forms of Switching Functions

- 부울 함수는 여러 가지 대수학적인 정리들을 이용하여 간략화 될 수 있다.
- 그러나 대수학적인 정리들을 이용한 간략화 방법은
  1. 체계적인 방법을 적용하기가 어렵다.
  2. 완전한 최소식을 얻지 못할 수도 있다.
- AND나 OR 게이트를 사용하여 함수를 회로로 구성하는 경우, 그 구현 비용은 게이트의 개수와 사용된 입력의 개수에 의존한다.
- 카르노맵 방식은 AND 와 OR 게이트로 이루어진 2단 회로를 최소비용으로 구현할 수 있도록 해준다.
- 그러므로 최소비용으로 2단 회로를 구성하기 위해서는 반드시 최소 논리곱의 합식이나 최소 논리합의 곱식을 찾아 내야 한다.

논리곱의 합식의  
논리 게이트 표현

  

논리합의 곱식의  
논리 게이트 표현



# Minimum Forms of Switching Functions

## ◆ 최소 논리곱의 합 (minimum sum of product)

- 다음 조건을 만족하는 논리 곱의 합 식으로 정의됨.
  - (a) 최소 수의 항들을 가진다.
  - (b) 각 항은 각각 최소 개수의 문자를 가진다.
- 또는 다음 조건을 만족하는 2단 게이트 회로에 해당됨.
  - (a) 최소 개수의 게이트 수를 가진다.
  - (b) 최소 개수의 게이트 입력을 가진다.
- 함수에 대한 최소항 전개와 달리,  
최소 논리곱의 합식은 반드시 하나인 것은 아니다.  
즉 주어진 함수는 같은 항의 수와 문자의 수를 가지는 두 가지 다른  
최소식을 가질 수 있다.

# Minimum Forms of Switching Functions

- 최소항 식이 주어졌을 때, 최소 논리곱의 합식은 다음 절차를 통해 구한다.
  - $XY' + XY = X$  정리를 이용하여 가능한 많은 문자들을 소거한다.
  - 합의 정리 등을 이용하여 여분의 중복항을 소거한다.
- 위 절차의 결과는 항을 결합하고 소거하는 순서에 의존하므로 얻어진 결과식이 반드시 최소식은 아니다.

예제)  $F(a, b, c) = \sum m(0, 1, 2, 5, 6, 7)$

$$F = a'b'c' + a'b'c + a'bc' + ab'c + abc' + abc$$

$$= a'b' + bc' + b'c + ab$$

$$F = a'b'c' + a'b'c + a'bc' + ab'c + abc' + abc$$


$$= a'b' + bc' + ac$$

# Two-and Three-variable Karnaugh Maps

## ◆ 2변수 카노맵

- 진리표와 마찬가지로, 카르노맵 역시 독립적인 변수 값들의 모든 가능한 조합을 각각의 사각형에 표현 가능하다.
- 2변수 함수  $F$ 에 대한 진리표와 이에 해당하는 카르노맵은 다음과 같다.


A	B	F
0	0	$m_0$
0	1	$m_1$
1	0	$m_2$
1	1	$m_3$

 


# Two-and Three-variable Karnaugh Maps

- 어떤 함수  $F$ 에 대한 진리표와 카르노맵은 아래와 같다.
- 카르노맵에서 각 1은  $F$ 의 최소항에 해당한다.
- 카르노맵에서 인접한 칸의 최소항들은 하나로 결합시킬 수 있다.

A	B	F
0	0	1
0	1	1
1	0	0
1	1	0

 

$$F = A'B' + A'B$$

 

$$F = A'B' + A'B$$

$$= A'$$

# Two-and Three-variable Karnaugh Maps

## ◆ 3변수 카르노맵

- 3변수 함수  $F$ 에 대한 진리표와 이에 해당하는 카르노맵은 다음과 같다.
- 3변수 카르노맵에서는 하나의 변수 값( $A$ )을 맵의 위에 기입하고
  - 다른 두 변수의 순서쌍( $B, C$ )을 맵의 왼쪽에 00, 01, 11, 10순으로 기입한다.
  - 각 조합에 대한  $F$ 값을 맵에 채워서 완성한다.

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

		A	
		0	1
BC	00	0	1
	01	0	0
	11	1	0
	10	1	1

# Two-and Three-variable Karnaugh Maps

- 다음은 3변수 카르노맵에서 최소항의 인접관계를 나타낸 그림이다.
- 물리적으로 인접하지 않아도 **한 변수의 값만 다르면 인접한 것으로 규정한다.**
- 각 인접항들은  $XY' + XY = X$ 를 이용하여 결합할 수 있다.

A \ BC		0	1
BC	00	000	100
	01	001	101
	11	011	111
	10	010	110

A \ BC		0	1
BC	00	000	100
	01	001	101
	11	011	111
	10	010	110

A \ BC		0	1
BC	00	000	100
	01	001	101
	11	011	111
	10	010	110

# Two-and Three-variable Karnaugh Maps

- 최소항 전개식에 대해 카르노맵에 표시하는 방법
  - 최소항 전개식 : 최소항에 대응하는 칸에 1, 나머지 칸에 0

A \ BC	BC	
	0	1
00	0	0
01	1	1
11	1	0
10	0	0

$$\begin{aligned}
 F(A, B, C) &= A'B'C + AB'C + A'BC \\
 &= \sum m(1, 3, 5)
 \end{aligned}$$

A \ BC	BC	
	0	1
00	1	0
01	0	0
11	0	1
10	1	1

$$\begin{aligned}
 F(A, B, C) &= A'B'C' + ABC + A'BC' + ABC' \\
 &= \sum m(0, 2, 6, 7)
 \end{aligned}$$


# Two-and Three-variable Karnaugh Maps

- 곱항을 카르노맵에 표시하는 방법의 예


$$F1 = A'BC + ABC + A'BC' + ABC'$$

$$F2 = A'BC' + ABC'$$


$$F3 = AB'C' + ABC'$$

 

$$B = x1x$$

 

$$BC' = x10$$

 

$$AC' = 1x0$$



# Two-and Three-variable Karnaugh Maps


- 함수의 대수식을 카르노맵에 표시하는 방법의 예

$$F(A, B, C) = A'B'C' + A'B'C + A'BC + A'BC' + AB'C + ABC'$$

$$= (A'B'C' + A'B'C + A'BC + A'BC') + (A'B'C + AB'C) + (ABC' + A'BC')$$

$$= (A'B'(C' + C) + A'B(C + C')) + (B'C(A' + A)) + ((A + A')BC')$$
 
$$= (A'(B' + B)) + (B'C) + (BC') = A' + B'C + BC'$$



# Two-and Three-variable Karnaugh Maps

- 카르노맵을 이용한 함수의 간략화 식 유도하는 방법
  1. 간략화 할 함수를 카르노맵에 작성한다.
  2. 인접항들을 결합한다(루프로 묶는다).
  3. 결합한 인접항들을 최소 논리곱의 합 식으로 표현한다.
- 보수 함수 경우 카르노맵의 0을 1로, 1을 0으로 대체하여 위 과정을 수행.

A \ BC	0	1
00	0	0
01	1	1
11	1	0
10	0	0

$$F = AB'C + A'B'C + A'BC$$

$$= \sum m(1, 3, 5)$$

A \ BC	0	1
00	0	0
01	1	1
11	1	0
10	0	0

$A'C$

$B'C$

$$F = A'C + B'C$$

A \ BC	0	1
00	1	1
01	0	0
11	0	1
10	1	1

$C'$

$AB$



$$F = AB'C' + A'B'C' + ABC$$

$$+ A'BC' + ABC' = C' + AB$$
  
# Two-and Three-variable Karnaugh Maps

- 카르노맵을 이용한 부울대수의 기본 정리 증명

$$XY + X'Z + YZ = XY + X'Z \quad (\text{컨센서스 이론})$$




# Two-and Three-variable Karnaugh Maps

- 함수가 둘 이상의 최소 논리곱의 합 식을 가진다면, 카르노맵을 통해서 모든 식을 간략화 할 수 있다.


$$F = A'B'C' + A'B'C + A'BC' + AB'C + ABC + ABC'$$

$$= A'B + BC' + AC$$

$$= A'C' + B'C + AB$$

 

$$F = A'B + BC' + AC$$

 

$$F = A'C' + B'C + AB$$

# Four-variable Karnaugh Maps

## ◆ 4변수 카르노맵

- 3변수 카르노맵과 마찬가지로 두 변수의 순서쌍 (AB, CD)을 각각 00, 01, 11, 10순으로 기입한다.

A	B	C	D	F
0	0	0	0	$m_0$
0	0	0	1	$m_1$
0	0	1	0	$m_2$
0	0	1	1	$m_3$
.	.	.	.	.
.	.	.	.	.
.	.	.	.	.
1	1	1	0	$m_{14}$
1	1	1	1	$m_{15}$

AB \ CD		00	01	11	10
CD	00	$m_0$	$m_4$	$m_{12}$	$m_8$
	01	$m_1$	$m_5$	$m_{13}$	$m_9$
	11	$m_3$	$m_7$	$m_{15}$	$m_{11}$
	10	$m_2$	$m_6$	$m_{14}$	$m_{10}$

# Four-variable Karnaugh Maps


- 다음은 4변수 카르노맵의 예.

$$(1) F = A'B'C'D' + A'BC'D' + ABC'D' + AB'C'D' + A'BC'D + A'BCD + ABCD + AB'CD + A'B'CD' + A'BCD' + ABCD' + AB'CD'$$

$$(2) F = A'BC'D' + ABC'D' + A'B'C'D + A'BC'D + ABC'D + A'B'CD + AB'CD'$$


$$F(A, B, C, D)$$

$$= A'B + AC + D'$$

 

$$F(A, B, C, D)$$

$$= BC' + A'B'D + AB'CD'$$

 

# Don't Care Input Combinations

❖ 함수  $F$ 의 특정 입력값이 출력값에 영향을 끼치지 않는 경우, 이때의 특정 입력조합을 무관항(don't care term)이라 한다.

❖ What if we know that **particular input combinations can never occur?**

- e.g., Minimize  $F = xy'z'$ , given that  $x'y'z'$  ( $xyz=000$ ) can *never* be true, and that  $xy'z$  ( $xyz=101$ ) **can never be true**
- So it **doesn't matter** what  $F$  outputs when  $x'y'z'$  or  $xy'z$  is true, because those cases *will never occur*
- Thus, make  $F$  be 1 or 0 for those cases *in a way that best minimizes the equation*

❖ On K-map

- Draw **Xs** for don't care combinations
  - Include **X** in circle **ONLY** if minimizes equation
  - Don't include other Xs

		$yz$		$y'z'$		
		00	01	11	10	
$x$	0	X	0	0	0	
	1	1	X	0	0	

Good use of don't cares

		$yz$		$y'z'$		unneeded
		00	01	11	10	
$x$	0	X	0	0	0	↓ $xy'$
	1	1	X	0	0	


Unnecessary use of don't cares; results in extra term

$$F = xy'z' = y'z' = xy'$$

# Optimization Example using Don't Cares
 
## ❖ Minimize:

- $F = \underline{a'bc'} + abc' + a'b'c$
- Given don't cares:  $a'bc$ ,  $abc$   
don't care mean that bc can never be 11
- $F = a'c + b$  : with two don't care Xs  
number of transistors:  $(2+0+2)*2=8$
- $F = a'b'c + bc'$  : without don't cares  
number of transistors:  $(3+2+2)*2=14$



$$F = a'c + b$$

## ❖ Note: Introduce don't cares with caution

- Must be *sure* that we really don't care what the function outputs for that input combination
- If we do care, even the slightest,  
then it's probably safer to set the output to 0




# Four-variable Karnaugh Maps

- 다음은 4변수 카르노맵을 이용한 함수 간략화의 예이다.


(좌)  $F_2(A, B, C, D) = \sum m(0, 2, 3, 5, 6, 7, 8, 10, 11, 14, 15)$

(우) 무관항을 포함한 4변수 카르노맵 예. 무관항은 필요할 경우에만 1로 사용.
 
$$F(A, B, C, D) = \sum m(1, 3, 5, 7, 9) + \sum d(6, 12, 13)$$



$$F_2(A, B, C, D) = C + B'D' + A'BD$$

 

$$F(A, B, C, D) = AD + C'D$$



# Automating Two-Level Logic Size Optimization

## ❖ Minimizing by hand

- Is hard for functions with 5 or more variables
- May not yield minimum cover depending on order we choose
- Is error prone
  
## ❖ Minimization thus typically done by automated tools

- **Exact algorithm** : finds optimal solution
- **Heuristic** : finds good solution, but not necessarily optimal



# Determination of Minimum Expressions Using Essential Prime Implicants


## ❖ 관련항(implicant)

- 카르노맵에서 1이 하나 있거나 루프로 묶여진 1들을 관련항이라 한다.
 
## ❖ 주항(prime implicant)

- 관련항 중에서 더 이상 다른 항과 결합될 수 없는 관련항을 주항이라 한다.

- ✓  $A'B'C'D'$ 는 주항이 아니다.
- ✓  $A'B'C$ ,  $A'CD'$ 는 주항이다.
- ✓  $ABC'$ 는 주항이 아니다.
- ✓  $AC'$ 는 주항이다.



# Determination of Minimum Expressions Using Essential Prime Implicants

- 어떤 함수의 최소 논리곱의 합 식은 몇 개의 주항으로 구성된다 (반드시 그런 것은 아니다).
- 카르노맵 상에서 최소 논리곱의 합 식을 찾기 위해서, 모든 1을 포함할 수 있는 최소 개수의 주항을 찾아야 한다.
- 무관항은 1로 취급하나 무관항으로 구성된 최소식은 인정하지 않는다.
- 모든 주항이 최소 논리곱의 합 식에 포함되는 것은 아니다.

		AB			
		00	01	11	10
CD	00		1	1	
	01	1	1	1	
	11	1		1	1
	10			1	1


모든 주항  
:  $A'B'D$ ,  $BC'$ ,  $AC$ ,  $A'C'D$ ,  $AB$ ,  $B'CD$

최소식  $F = A'B'D + BC' + AC$

# Determination of Minimum Expressions Using Essential Prime Implicants
 
## ◆ 필수주항(essential prime implicant)

- 하나의 최소항이 단 하나의 주항에만 포함되면 이 주항을 필수주항이라 한다.
- 필수주항은 최소 논리곱의 합 식에 포함시켜야 한다.




모든 주항  
:  $BD$ ,  $B'C$ ,  $AC$ ,  $CD$

$A'BC'D$ ,  $A'B'CD'$ ,  $ABCD'$ 는 각각  $BD$ ,  $B'C$ ,  $AC$ 에만 포함되므로 필수주항이다.

따라서,  
최소식  $F = BD + B'C + AC$
 
## Determination of Minimum Expressions Using Essential Prime Implicants

- 카르노맵에서 최소 논리곱의 합 식을 찾기 위해  
먼저 모든 필수주항을 루프로 묶어야 한다.
- 아직 포함되지 않은 1이 단 하나의 주항에 포함되면 그 주항은 필수주항
- 주어진 최소항과 인접한 모든 1이 단 하나의 항에 포함되면  
그 항은 필수주항(인접한 무관항도 1로 취급)



$A'B'C'D$ 와 인접한  $A'B'C'D'$ ,  $A'BC'D$ 는 모두  $A'C'$ 에 포함되므로  $A'C'$ 는 필수주항

마찬가지로  $A'B'CD'$ 에 대해서는  $A'B'D'$ ,  $AB'CD$ 에 대해서는  $ACD$ 가 필수주항

따라서 F의 최소 논리곱의 합 식은  
 $A'C' + A'B'D' + ACD + A'BD$ (or  $BCD$ )

# Determination of Minimum Expressions Using Essential Prime Implicants

- 카르노맵에서 최소 논리곱의 합 식을 찾기 위한 과정은 다음과 같다.
  1. 아직 루프로 묶여진 항에 포함되지 않은 최소항(하나의 1)을 선택
  2. 이 최소항에 인접하는 모든 1과 x를 찾는다.(n-변수 맵에서는 n개)
  3. 하나의 단일 항이 이 최소항과 인접한 모든 1과 x를 포함할 때,  
이 단일 항은 필수주항이므로 이 단일 항을 선택
  4. 모든 필수주항이 선택될 때까지 과정 1, 2, 3 반복
  5. 나머지 1을 포함하는 주항의 최소 집합을 찾음.


## Other Uses of Karnaugh Maps

- 식의 인수화를 쉽게 할 수 있다.

첫 행의 두 항은  $A'B'$ 를 공통으로 가지고 있다.  
두 항은  $A'B'(C' + D)$ 로 표현 할 수 있다.

나머지 두 항은  $AC$ 를 공통으로 가지고 있다.  
두 항은  $AC(B + D')$ 로 표현 할 수 있다.

함수 F 이들 항의 합으로 표현 할 수 있다.

 

$$F = A'B'(C' + D) + AC(B + D')$$